



MAASAI MARA UNIVERSITY

**REGULAR UNIVERSITY EXAMINATIONS
2018/2019 ACADEMIC YEAR
SECOND YEAR SECOND SEMESTER**

**SCHOOL OF SCIENCE
UNIVERSITY EXAMINATIONS FOR THE DEGREE OF
BACHELOR OF SCIENCE AND BACHELOR OF
EDUCATION SCIENCE**

**COURSE CODE: PHY 2213
COURSE TITLE: ELECTRICAL CIRCUITS**

DATE: 16TH APRIL, 2019

TIME: 0830-1030 HRS

INSTRUCTIONS

- Answer Question **ONE** and any other **TWO**.
- Use of sketch diagrams where necessary and brief illustrations are encouraged.
- Read the instructions on the answer booklet keenly and adhere to them.


This paper consists of 4 printed pages.

QUESTION ONE:

[30]

- a) State three advantages of connecting loads in parallel to series in electrical circuits. [3]
- b) Explain the term 'network' as used in electrical circuits. [2]
- c) Find the instantaneous circuit current if a voltage $v = 100\sin(1000t)$ V is applied to:
 - (i) a pure resistive circuit of $R=50 \Omega$ [2]
 - (ii) a pure inductive circuit of $L=0.02$ H [3]
 - (iii) a pure capacitive circuit of $C=10 \mu\text{F}$ [3]
- d) By Superposition Principle find P_R in figure 1. [3]

Figure 1

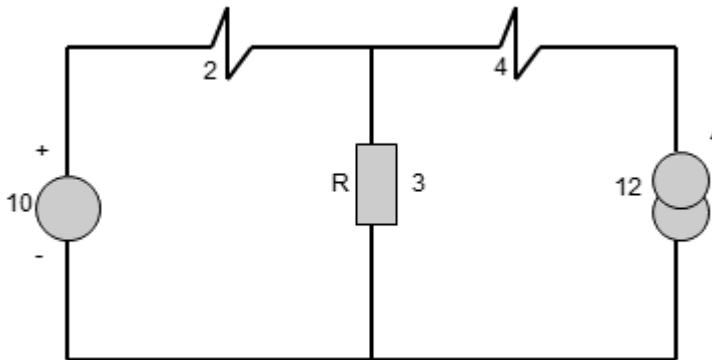


- e) Explain the difference between active and passive power. [4]
- f) Find the current phasor if a $60 \text{ Hz } 220 \angle 30^\circ$ V ac voltage is applied to
 - (i) a pure resistive circuit of $R=10 \Omega$ [2]
 - (ii) a pure inductive circuit of $L=0.2$ H [2]
 - (iii) a pure capacitive circuit of $C=10 \mu\text{F}$ [2]
- g) State the following theorems:
 - (i) Norton's theorem states [2]
 - (ii) Thevenin's theorem [2]

QUESTION TWO: [20]


a) Show that for the circuit shown on fig.2 , Current lags voltage by 90° [4]

Figure 2

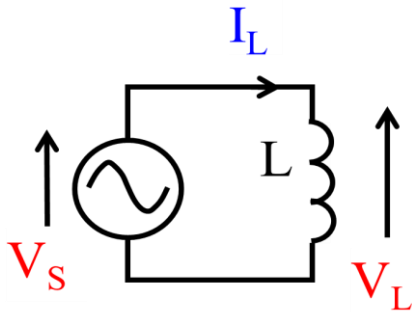

b) Refer to the circuit of Fig 3, find:
 (i) the total impedance, Z_T [7]
 (ii) the supply current, I_T [3]
 (iii) the branch currents, I_1, I_2 and I_3 . [6]

Figure 3

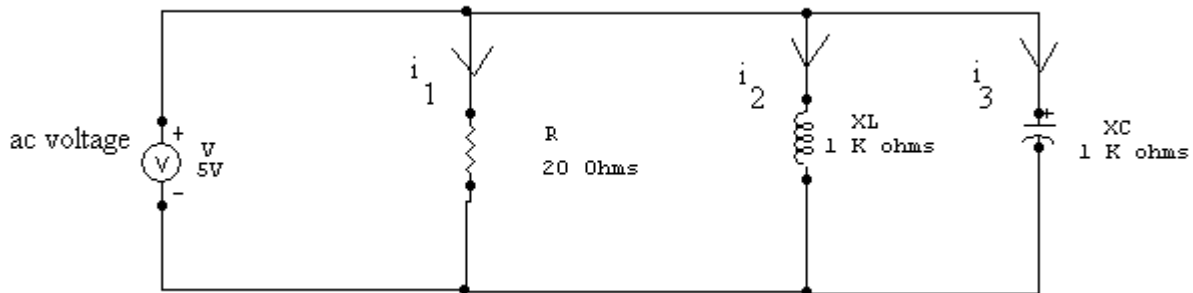

QUESTION THREE: [20 marks]

a) Explain the following
 (i) Capacitive reactance [2]
 (ii) Inductive reactance [2]
 (iii) Impedance [2]
 (iv) Phasor [2]


b) An rms voltage of 10.0 V with a frequency of 1.00 kHz is applied to a 0.395-mF capacitor.

- (i) What is the rms current in this circuit? [3]
- (ii) By what factor does the current change if the frequency of the voltage is doubled? [1]
- (iii) Calculate the current for a frequency of 2.00 kHz. [1]

c) For the circuit in fig.4

- (i) Compute P_T and Q_T for the following circuit. [5]
- (ii) Reduce the circuit to its simplest form [2]


Figure 4

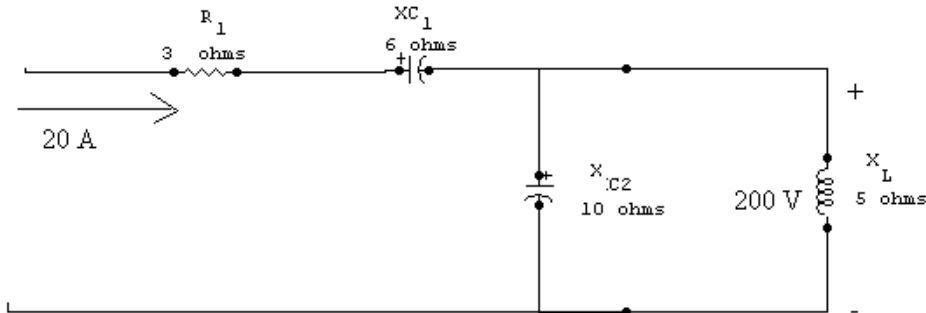

QUESTION FOUR: [20 marks]

- a) Explain the steps involved in applying the Mesh Analysis in solving electric circuits [5]
- b) Use Mesh Analysis in fig 5 to find:
 - (i) The current i through resistor R . [7]
 - (ii) Power through resistor R . [3]

Figure 5

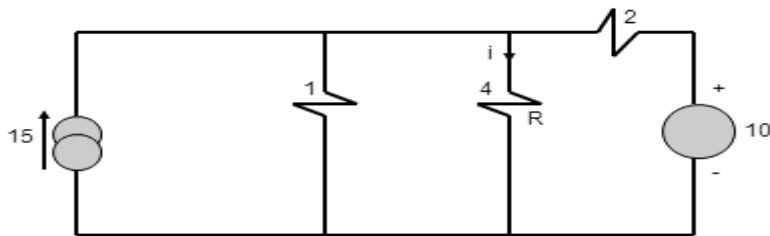

- d) Explain the procedure for the application of the Millman's Theorem [5]

//End//