



# MAASAI MARA UNIVERSITY

**REGULAR UNIVERSITY EXAMINATIONS  
2018/2019 ACADEMIC YEAR  
SECOND YEAR SECOND SEMESTER**

**SCHOOL OF SCIENCE  
UNIVERSITY EXAMINATIONS FOR THE  
DEGREE OF BACHELOR OF SCIENCE AND  
BACHELOR OF EDUCATION SCIENCE**

**COURSE CODE: PHY 2213  
COURSE TITLE: ELECTRICAL CIRCUITS**

**DATE: 16<sup>TH</sup> APRIL, 2019**

**TIME: \_\_0830-1030 HRS**

---

## **INSTRUCTIONS**

- Answer Question **ONE** and any other **TWO**.
- Use of sketch diagrams where necessary and brief illustrations are encouraged.
- Read the instructions on the answer booklet keenly and adhere to them.


**This paper consists of   4   printed pages.**

**QUESTION ONE:**

**[30]**

- a) State three advantages of connecting loads in parallel to series in electrical circuits. [3]
- b) Explain the term 'network' as used in electrical circuits. [2]
- c) Find the instantaneous circuit current if a voltage  $v = 100\sin(1000t)$  V is applied to:
  - (i) a pure resistive circuit of  $R=50 \Omega$  [2]
  - (ii) a pure inductive circuit of  $L=0.02$  H [3]
  - (iii) a pure capacitive circuit of  $C=10 \mu\text{F}$  [3]
- d) By Superposition Principle find  $P_R$  in figure 1. [3]

Figure 1

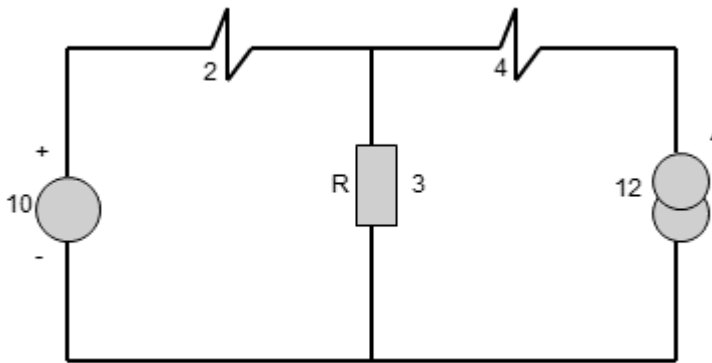


- e) Explain the difference between active and passive power. [4]
- f) Find the current phasor if a 60 Hz  $220\angle 30^\circ$  V ac voltage is applied to
  - (i) a pure resistive circuit of  $R=10 \Omega$  [2]
  - (ii) a pure inductive circuit of  $L=0.2$  H [2]
  - (iii) a pure capacitive circuit of  $C=10 \mu\text{F}$  [2]
- g) State the following theorems:
  - (i) Norton's theorem states [2]
  - (ii) Thevenin's theorem [2]

**QUESTION TWO:**

**[20]**


- a) Show that for the circuit shown on fig.2 , Current lags voltage by  $90^\circ$  [4]

Figure 2

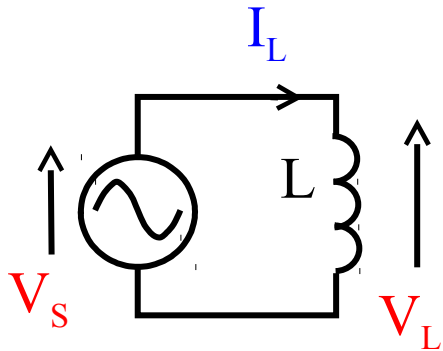

- b) Refer to the circuit of Fig 3, find:
- (i) the total impedance,  $Z_T$  [7]
  - (ii) the supply current,  $I_T$  [3]
  - (iii) the branch currents,  $I_1$ ,  $I_2$  and  $I_3$ . [6]

Figure 3

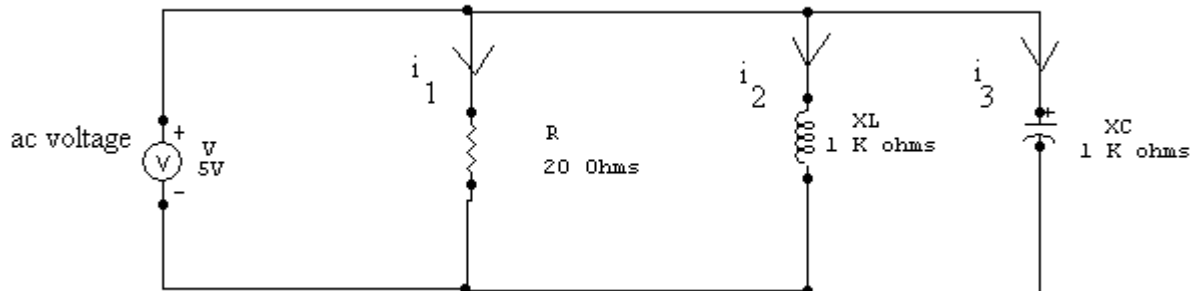

**QUESTION THREE:**

**[20 marks]**

- a) Explain the following
- (i) Capacitive reactance [2]
  - (ii) Inductive reactance [2]
  - (iii) Impedance [2]
  - (iv) Phasor [2]


**b)** An rms voltage of 10.0 V with a frequency of 1.00 kHz is applied to a 0.395-mF capacitor.

- (i) What is the rms current in this circuit? [3]
- (ii) By what factor does the current change if the frequency of the voltage is doubled? [1]
- (iii) Calculate the current for a frequency of 2.00 kHz. [1]

**c)** For the circuit in fig.4

- (i) Compute  $P_T$  and  $Q_T$  for the following circuit. [5]
- (ii) Reduce the circuit to its simplest form [2]


Figure 4

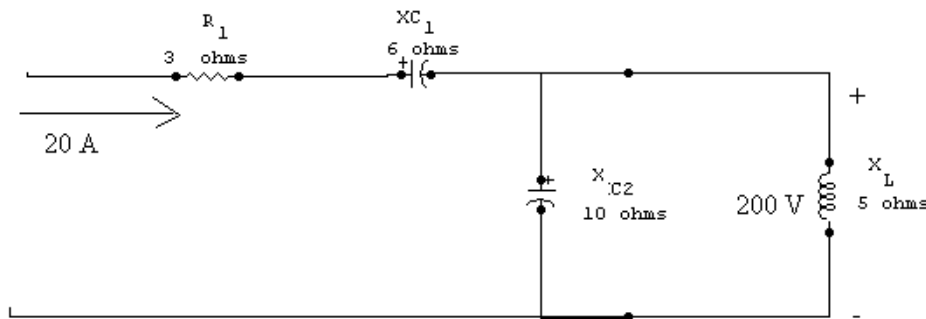

**QUESTION FOUR: [20 marks]**

- a) Explain the steps involved in applying the Mesh Analysis in solving electric circuits [5]
- b) Use Mesh Analysis in fig 5 to find:
  - (i) The current  $i$  through resistor  $R$ . [7]
  - (ii) Power through resistor  $R$ . [3]

Figure 5

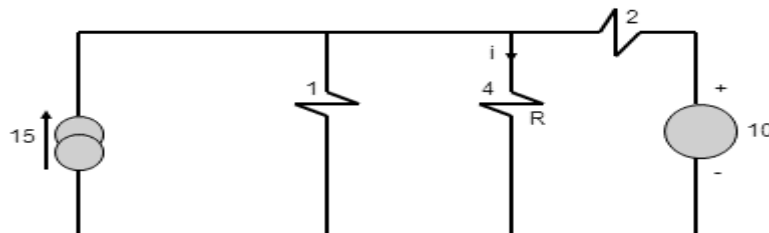

**d)** Explain the procedure for the application of the Millman's Theorem [5]

**//End//**