



# MAASAI MARA UNIVERSITY

REGULAR UNIVERSITY EXAMINATIONS  
2023/2024 ACADEMIC YEAR  
THIRD YEAR FIRST SEMESTER

SCHOOL OF PURE, APPLIED AND HEALTH  
SCIENCES

DEPARTMENT OF MATHEMATICS AND  
PHYSICAL SCIENCES  
BACHELOR OF SCIENCE (PHYSICS)

**COURSE CODE: PHY 3115-1**

**COURSE TITLE: PHYSICS LABORATORY V**

**DATE: 4/6/ 2023**

**TIME: 0830 - 1030 HRS**

**INSTRUCTIONS**

- 1 Answer question **ONE** and any other **TWO** questions in **section B**
- 2 Use of sketch diagrams where necessary and brief illustrations are encouraged.
- 3 Read the instructions in the answer booklet keenly and adhere to them.
- 4 *This paper contains **FOUR** printed pages (please turnover).*

## SECTION A

### QUESTION ONE (20 MARKS)

- a) Define the following terms
- i) Interference (1mk)
  - ii) Reflection (1mk)
- b) A common base transistor amplifier has an input resistance of  $20\ \Omega$  and an output resistance of  $100\ \text{k}\Omega$ . The collector load is  $1\ \text{k}\Omega$ . If a signal of  $500\ \text{mV}$  is applied between the emitter and base, find the voltage amplification. Assume  $\alpha_{ac}$  to be 1. (4mks)
- c) An n-p-n transistor at room temperature has its emitter disconnected. A voltage of  $5\ \text{V}$  is applied between the collector and base. With collector positive, a current of  $0.2\ \mu\text{A}$  flows. When the base is disconnected and the same voltage is applied between the collector and emitter, the current is found to be  $20\ \text{M}$  when the collector current is  $1\ \text{mA}$ .
- i)  $\alpha$ , (2mks)
  - ii)  $I_E$  (2mks)
  - iii)  $I_B$  (2mks)
- d) In the Michelson interferometer, three conditions are essential to obtain interference fringes. State them. (3mks)
- e) Through what distance must the movable mirror of a Michelson interferometer be displaced for 4500 fringes of red cadmium line to cross the center of the field of view given that the wavelength of the source is  $6550 \times 10^{-10}\ \text{m}$  (3mks)
- f) State **TWO** conditions for interference (2mks)

## SECTION B

### QUESTION TWO (10 MARKS)

- a) State **THREE** applications of JFETs (3mks)
- b) List **TWO** advantages of FETs over BJTs (2mks)
- c) With the help of diagrams differentiate between an N-channel and a P-channel JFET. (2mks)
- d) Explain **THREE** differences between MOSFETs and BJTs (3mks)

### QUESTION THREE (10 MARKS)

a) An NPN transistor is used in a switching circuit as shown in figure 1 below. Given that Beta value=125,  $R_L = 700 \Omega$ ,  $R_B = 50 K\Omega$  and  $V_{CE} = 0$ .

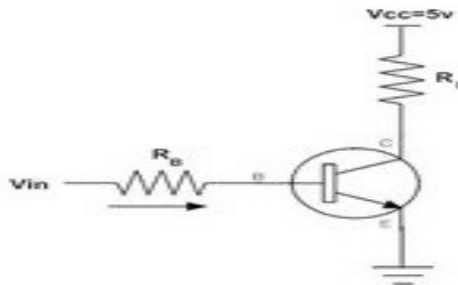


Figure 1

Calculate

- Collector current  $I_C$  (2mks)
  - Base Current  $I_B$  (2mks)
- b) With the help of diagrams, briefly describe three types of NPN or PNP transistor configurations. (6mks)

### QUESTION FOUR (10 MARKS)

a) In a laboratory experiment Gilbert arranged his apparatus as shown in Figure 2 below;

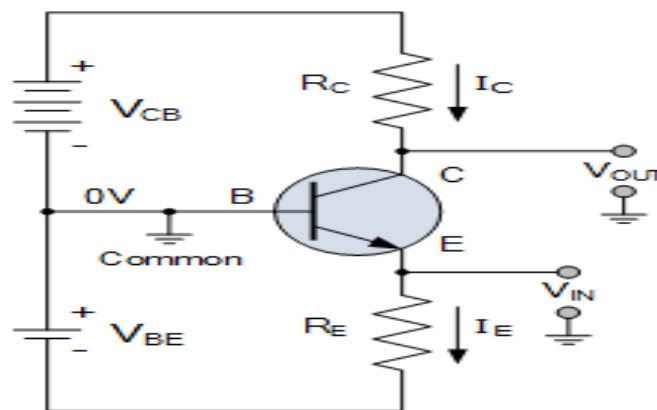


Figure 2.

Study the diagram and answer the questions that follow

- With a reason name the type of transistor configuration above (1mk)
- In terms of doping differentiate between the parts labelled B, E and C (3mks)

iii) Gilbert realized that the amplification factor of the circuit above is unity. For a reason explain another transistor configuration connection that you would suggest to him in order to amplify small AC signals better.

**(2mks)**

**b)** In a common base connection, the emitter current is 1mA. If the emitter circuit is open, the collector current is 50  $\mu$ A. Find the total collector current.

Given that  $\alpha = 0.92$ .

**(2mks)**

**c)** In Young's double-slit experiment, why do we use monochromatic light? if white light is used, how would the pattern change? **(2mks)**

**/END/**