



# **MAASAI MARA UNIVERSITY**

**REGULAR UNIVERSITY EXAMINATIONS**

**2023/2024 ACADEMIC YEAR**

**SECOND YEAR SECOND SEMESTER**

**SCHOOL OF PURE, APPLIED AND HEALTHY  
SCIENCES**

**MASTER OF SCIENCE IN PHYSICS  
(ELECTRONICS)**

**COURSE CODE: PHY 8210**

**COURSE TITLE: INTEGRATED ELECTRONICS**

**DATE: 30/1/2024**

**TIME: 0830-1130 HRS**

---

## **INSTRUCTIONS TO CANDIDATES**

1. Answer Question **ONE** and any other **Two** questions

*This paper consists of **four** printed pages. Please turn over.*

**Question One [30 Marks]**

- (a) State and explain two main problems which face designers who have to integrate analog and digital circuits on the same PCB (printed circuit board). [4marks]
- (b) Sketch a neat diagram of an NPN transistor circuit configuration for use in a digital circuit. [3marks]
- (c) Explain the main drawback of the analog circuits. [2marks]
- (d) State two noncomputer applications of digital circuits. [2marks]
- (e) Draw a well labelled circuit of basic Sample-and-Hold amplifier. [4marks]
- (f) State three applications of a high-speed analog-to-digital converter. [3marks]
- (g) Differentiate between digital to analog converters and analog to digital converters. [4marks]
- (h) Explain two advantages of implementing a lock-in amplifier using digital technologies [4marks]
- (i) Explain two advantages of digital circuit over analog circuit. [4marks]  
is accurate and much more immune to noise problems.

**QUESTION TWO [20 MARKS]**

- (a). (i) State two examples of digital computer circuits [2marks]
- (ii) Discuss the operation of a digital circuit. [4marks]
- (b) State and explain two sources of electronic noise. [4marks]
- (c) Find the network function  $V_2 / V_1$  in the circuits shown in Fig.
  - (i) 1 (a) [3marks]
  - (ii) 1 (b) [3marks]

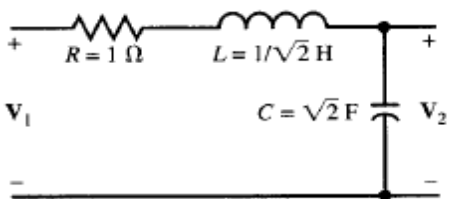


Fig 1 (a)

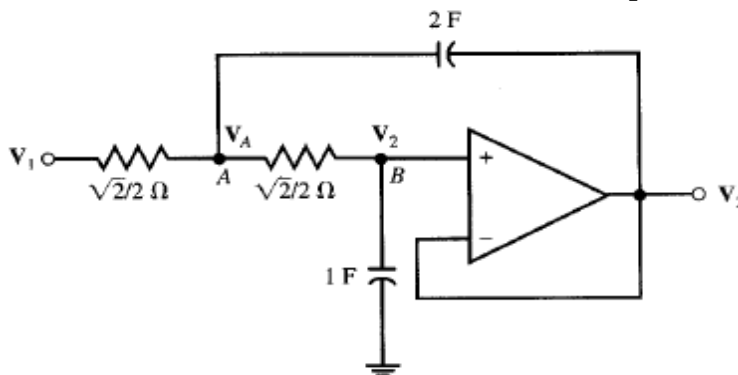


Fig. 1 (b)

- (d) With suitable circuit diagrams, differentiate between a low pass filter and a high pass filter [4marks]

**QUESTION THREE [20MARKS]**

- (a) Draw a circuit diagram of a Schmitt trigger [3marks]
- (b) What is an Analog comparator? Explain its working principle. [5marks]
- (c) Explain two types of the analog circuit based on the circuit behavior and the components used. [4marks]
- (d) Briefly explain the basic operation of a Sample and Hold Amplifier. [4marks]
- (e) State four analog physical quantities found in nature. [4marks]

**QUESTION FOUR [20MARKS]**

- (a) State and explain the successive approximation A–D converter [4marks]
- (b) Discuss two applications of DACs and ADCs [4marks]
- (c) Draw a block diagram of a triangular wave generator. Explain how it works. [4marks]
- (d) Define the term 555 timers as used in electronics. [2marks]
- (e) State and explain three differences between analog and digital circuits. [6marks]

**QUESTION FIVE [20MARKS]**

- (a) Explain two advantages of a binary system [4marks]
- (b) Draw a well-labelled diagram of:  
(i) the block diagram of a counter-ramp and a successive approximation A–D converter. [4marks]  
(ii) the analog waveforms in a counter-ramp A–D converter. [3marks]  
(iii) the analog waveforms in a successive approximation A–D converter. [3marks]
- (c) Describe the operation of an analog comparators. [4marks]
- (d) Differentiate between square and triangular wave generators [2marks]

/END/